True table

	Binary 4-Bit					Seç	gmei	nt 1					Seç	gme	nt 2			
	3A	2B	1C	0D	a ₁	b ₁	C ₁	d ₁	e 1	f ₁	g ₁	a ₂	b ₂	C ₂	d ₂	e ₂	f ₂	g ₂
0	0	0	0	0	1	1	1	1	1	1	0	1	1	1	1	1	1	0
1	0	0	0	1	1	1	1	1	1	1	0	0	1	1	0	0	0	0
2	0	0	1	0	1	1	1	1	1	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	1	1	0	1	1	1	1	0	0	1
4	0	1	0	0	1	1	1	1	1	1	0	0	1	1	0	0	1	1
5	0	1	0	1	1	1	1	1	1	1	0	1	0	1	1	0	1	1
6	0	1	1	0	1	1	1	1	1	1	0	0	0	1	1	1	1	1
7	0	1	1	1	1	1	1	1	1	1	0	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	1	1	0	1	1	1	0	0	1	1
10	1	0	1	0	0	1	1	0	0	0	0	1	1	1	1	1	1	0
11	1	0	1	1	0	1	1	0	0	0	0	0	1	1	0	0	0	0
12	1	1	0	0	0	1	1	0	0	0	0	1	1	0	1	1	0	1
13	1	1	0	1	0	1	1	0	0	0	0	1	1	1	1	0	0	1
14	1	1	1	0	0	1	1	0	0	0	0	0	1	1	0	0	1	1
15	1	1	1	1	0	1	1	0	0	0	0	1	0	1	1	0	1	1

KV-Diagrams

a₁/ d₁	А		A	Ā		
В	0	0	1	1	\overline{D}	
	0	0	1	1	1	
<u> </u>	1	0	1	1	D	
\bar{B}	1	0	1	1	\overline{D}	
	Ē	()	Ē		

$$a_1 = d_1 = e_1 = f_1 = \overline{A} + \overline{B}\overline{C}$$

b ₁ / C ₁	А		Ä		
D	1	1	1	1	\overline{D}
В	1	1	1	1	2
	1	1	1	1	D
\bar{B}	1	1	1	1	\overline{D}
	\bar{c} C			Ē	

$$b_1=c_1=A+\overline{A}$$

a ₂	P	4	Ä		
Ь	1	0	0	0	\overline{D}
В	1	1	1	1	7
<u></u>	1	0	1	0	D
\bar{B}	1	1	1	1	\overline{D}
,	Ē	(2	Ē	

$$a_2 = A\overline{C} + BD + \overline{B}\overline{D} + \overline{A}\overline{B}C$$

C ₂	А		Å		
Б	0	1	1	1	\overline{D}
В	1	1	1	1	2
<u> </u>	1	1	1	1	D
\bar{B}	1	1	0	1	\overline{D}
	Ē	(Ē	

$$c_2 = D + \overline{A}\overline{C} + BC + A\overline{B}$$

e ₂	А		$ar{A}$		
	1	0	1	0	\overline{D}
В	0	0	0	0	7
Ē	0	0	0	0	D
В	1	1	1	1	\overline{D}
	Ē	(Ē	

$$e_2 = \overline{B}\overline{D} + \overline{A}\overline{D}C + \overline{C}\overline{D}A$$

b ₂	А		Ā		
_	1	1	0	1	\overline{D}
В	1	0	1	0	7
<u> </u>	1	1	1	1	D
\bar{B}	1	1	1	1	\overline{D}
<u>, </u>	Ē	$\bar{\mathcal{C}}$		Ē	

$$b_2 = \overline{B} + A\overline{C} + CD\overline{A} + \overline{C}\overline{D} + AB\overline{D}$$

d ₂	А		A		
_	1	0	1	0	\overline{D}
В	1	1	0	1	7
Ē	0	0	1	0	D
\bar{B}	1	1	1	1	\overline{D}
	Ē	\bar{C}		Ē	

 $d_{2} = \overline{D}\overline{B} + \overline{A}\overline{B}C + ABD + AB\overline{C} + BD\overline{C} + \overline{A}\overline{D}C$

f ₂	А		A		
Б	0	1	1	1	\overline{D}
В	0	1	0	1	2
Ē	1	0	0	0	D
В	1	1	0	1	\overline{D}
	\bar{c}			Ē	

$$f_2 = \overline{A}\overline{D}B + ABC + \overline{A}\overline{C}B + \overline{C}\overline{B}A + \overline{B}\overline{D}A + \overline{B}\overline{C}\overline{D}$$

g ₂	P	4	A		
Ь	1	1	1	1	\overline{D}
В	1	1	0	1	2
<u></u>	1	0	1	0	D
\bar{B}	1	0	1	0	\overline{D}
	$\bar{\mathcal{C}}$ C		5	Ē	

 $g_2 = AB + B\overline{D} + B\overline{C} + C\overline{A}B + A\overline{C}$